


Design & Layout of Dynamic CMOS logic circuit

BY SATYAKI CHAKRAVORTY


Given logic: $(AB + C(D + E))'$

Dynamic style used : Zipper Style

Circuit Diagram

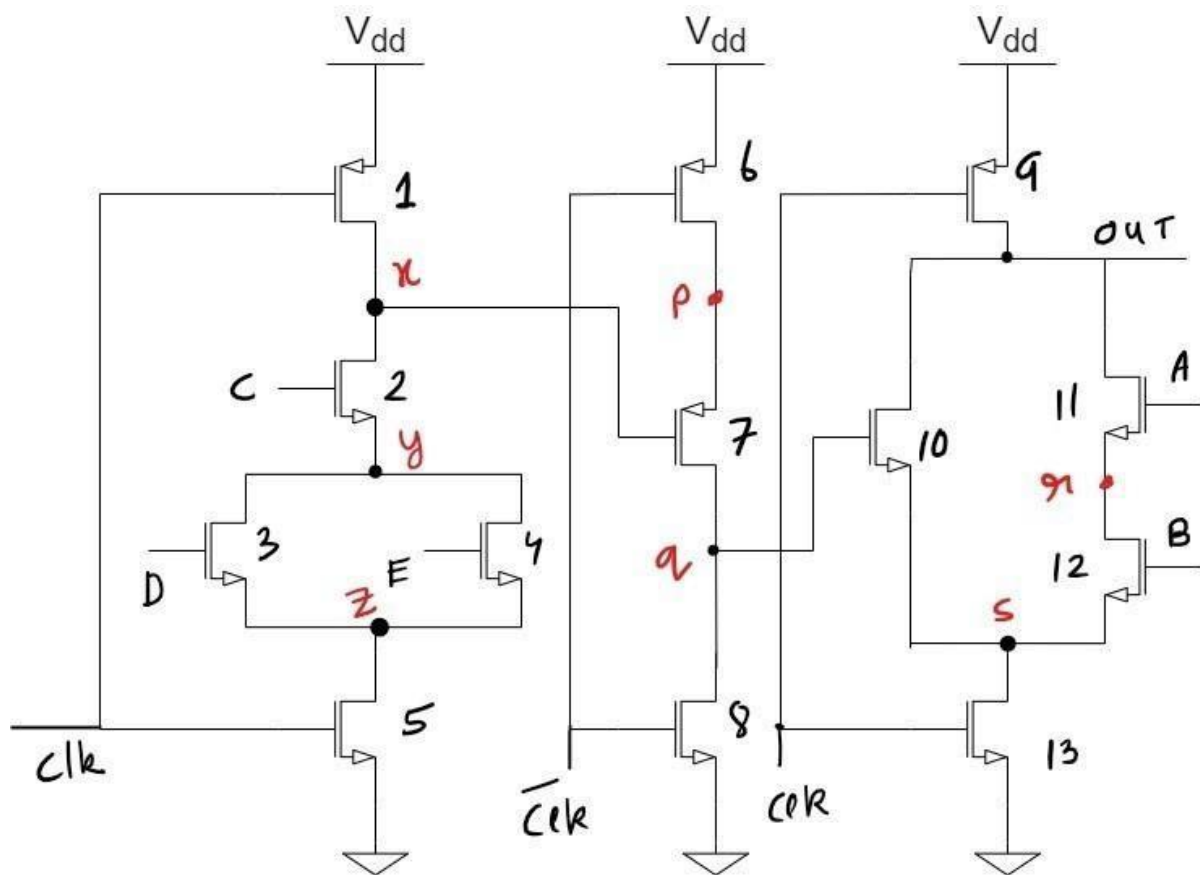

PRE-LAYOUT SIMULATION

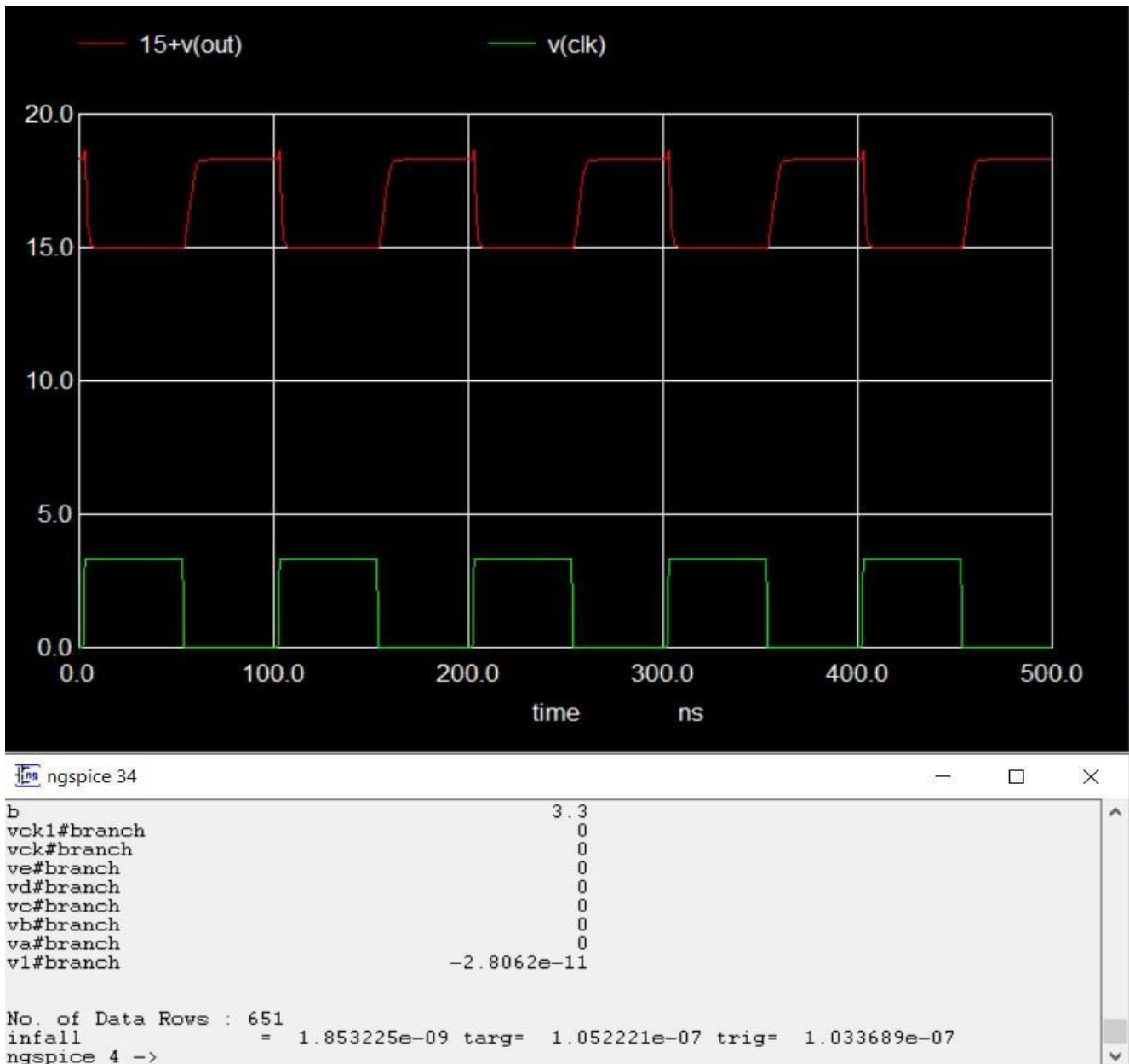


For Max frequency of operation, input vector chosen:


A=1, B=1, C=0, D=x, E=x as this corresponds to the worst-case condition.

$$\text{Max Freq} = 1/\text{infall} = \mathbf{539.6 \text{ MHz}}$$

LAYOUT OF THE CIRCUIT

 

POST-LAYOUT SIMULATION

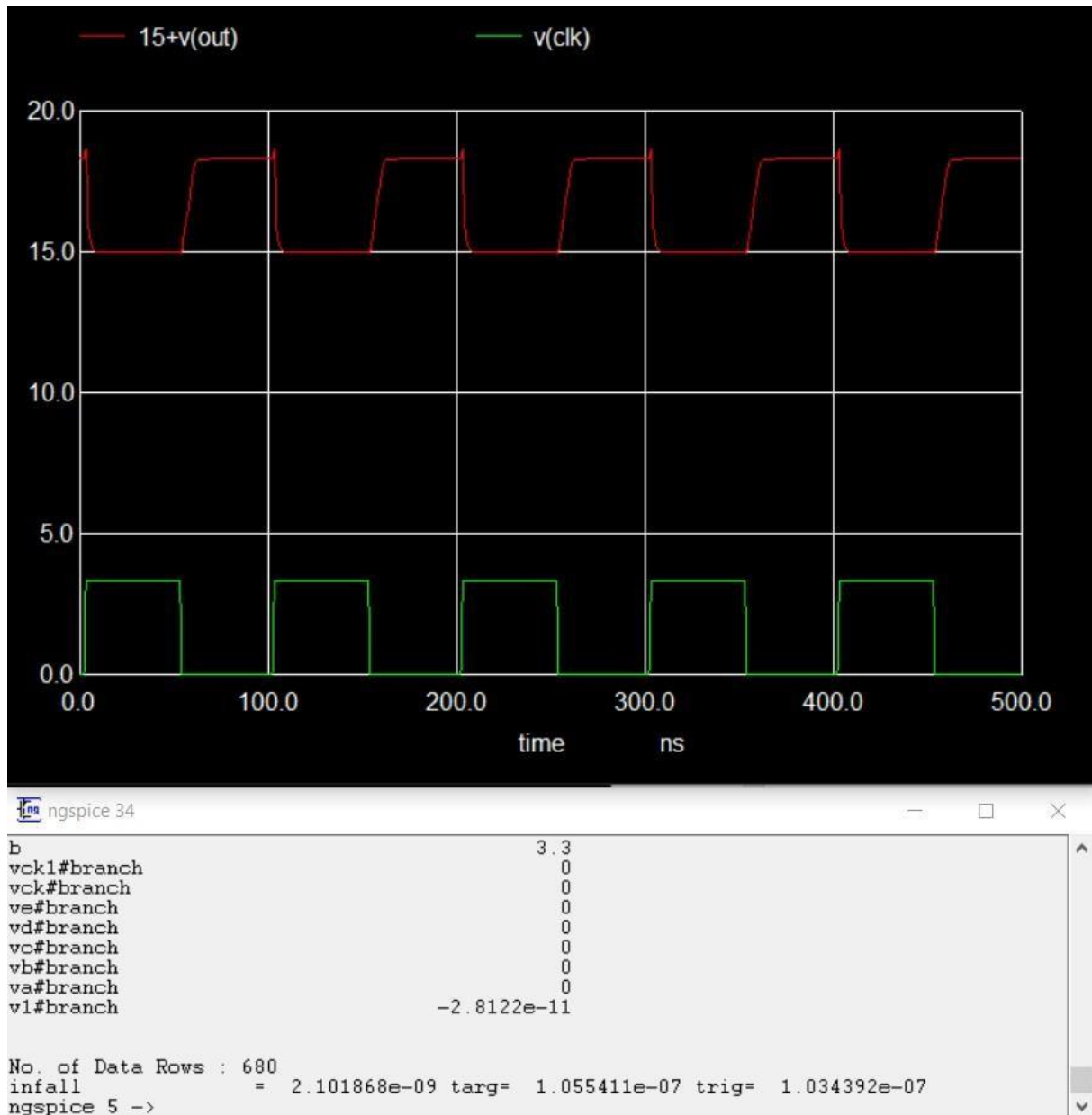

For Max frequency of operation, input vector chosen:

A=1,B=1 , C=0, D=x , E=x as this corresponds to the worst case condition.

$$\text{Max Freq} = 1/\text{infall} = \mathbf{475.7826 \text{ MHz}}$$

Thus, We can operate at a higher frequency for the pre-simulation case.